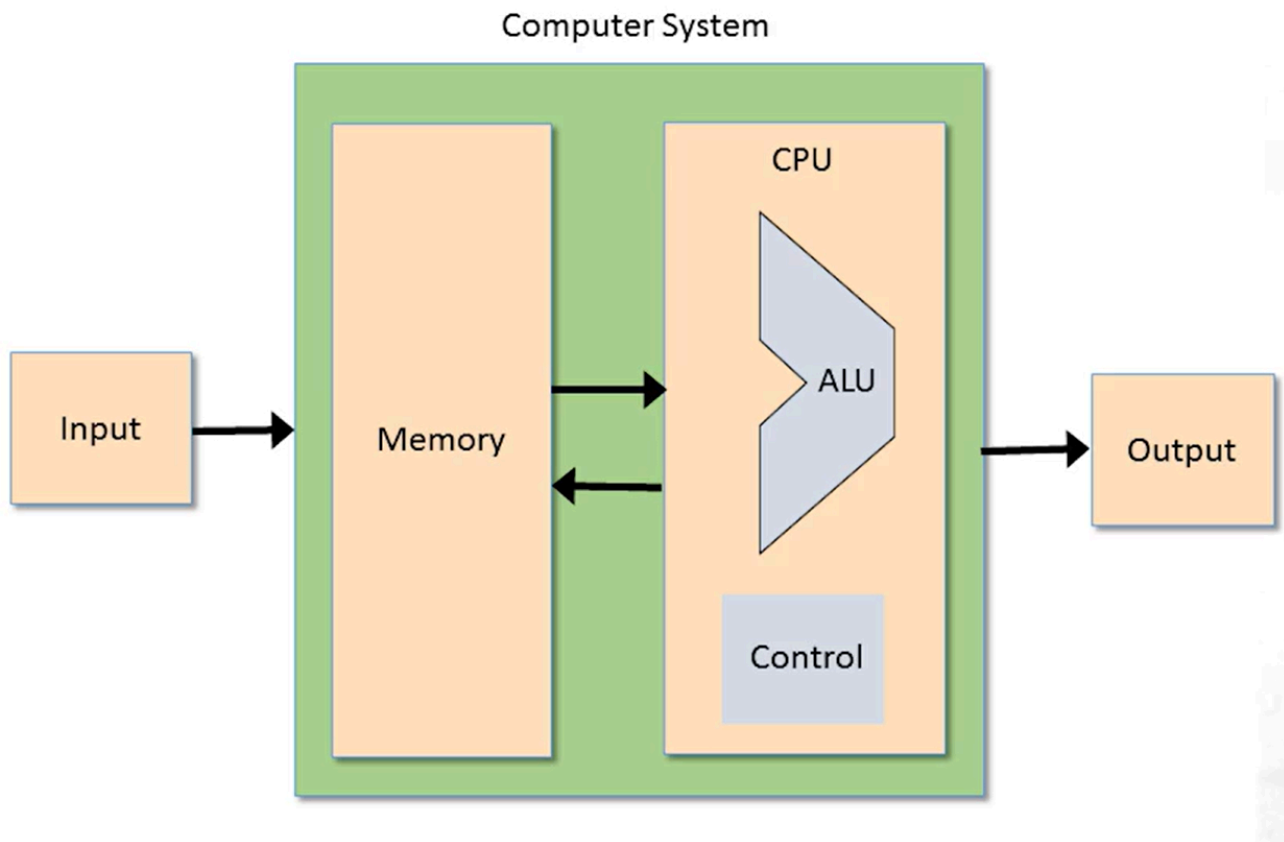


Module 2 - Binary and Arithmetic Logic Unit (ALU)


Von Neumann Architecture



Hack ALU

- Operates on two 16-bit, two's complement values
- Output a 16-bit, two's complement value
- Which function to compute is set by 6 1-bit inputs
- Computes one out of a family of 18 functions

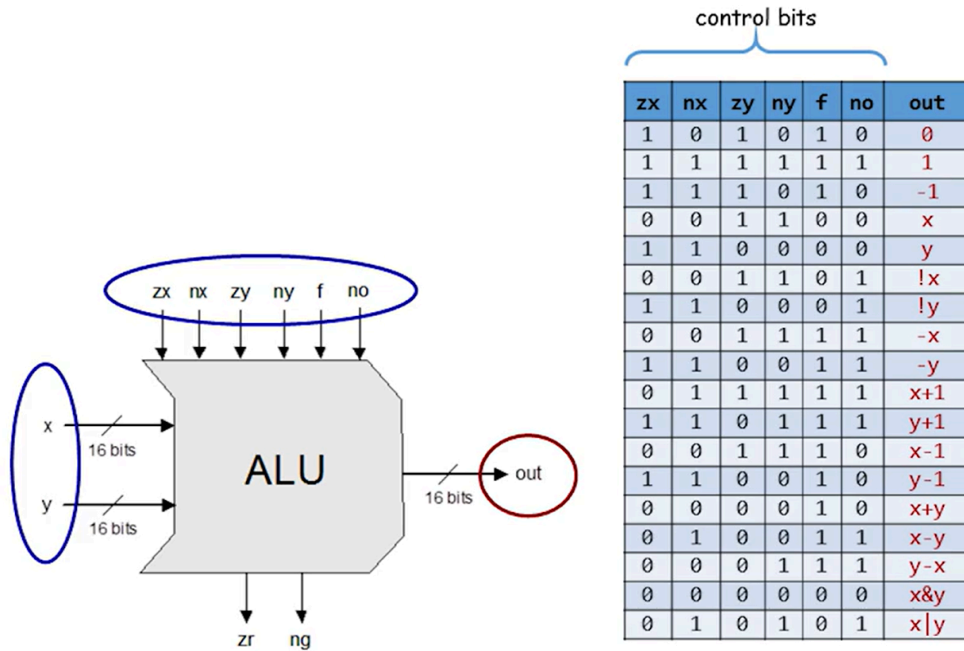- Also compute two 1-bit control outputs (zr and ng)



- Control bits:

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=

- The operations are performed from left to right.
- zx, zy is zero x or y respectively
- nx, ny is negate x or y respectively
- f is function
- no is negate output
- Output control bits
 - zr is 1 if output is zero
 - ng is 1 if output is negative